

Boolean Logic & Logic Gates III

Lecture 6



Lecture 6

Boolean Logic & Logic Gates III

KARNAUGH MAPPING



Karnaugh Maps

- Shortform : **K-map**
- Another **way of minimising** Boolean equations
 - Instead of simplification using Boolean algebra,
 - **Visual way** of simplification
 - **Recognising pattern** in the equation
- Came up by Edward Veitch in 1952
 - Veitch Diagram
 - Redefined by Maurice Karnaugh in 1953



Karnaugh Mapping

- Able to simplify a boolean equation once it's in its SOP form
- Example: $X = A'B'C + A'B'C' + A'BC'$

Only 1 input
changes
between
rows &
columns

	C'	C
A'B'	1	1
A'B	1	
AB		
AB'		

	C'	C
A'B'	1	1
A'B	1	
AB		
AB'		

- Final Equation : $X = A'B' + A'C'$



Karnaugh Mapping

- Let's try this now
 - $X = A'B'C' + A'B + ABC' + AC$



Karnaugh Mapping

- Let's try this now
 - $X = A'B'C' + A'B + ABC' + AC$

	C'	C
A'B'	1	
A'B	1	1
AB	1	1
AB'		1

	C'	C
A'B'	1	
A'B	1	1
AB	1	1
AB'		1


	C'	C
A'B'	1	
A'B	1	1
AB	1	1
AB'		1

– Final Equation : $X = A'C' + B + AC$




Karnaugh Mapping

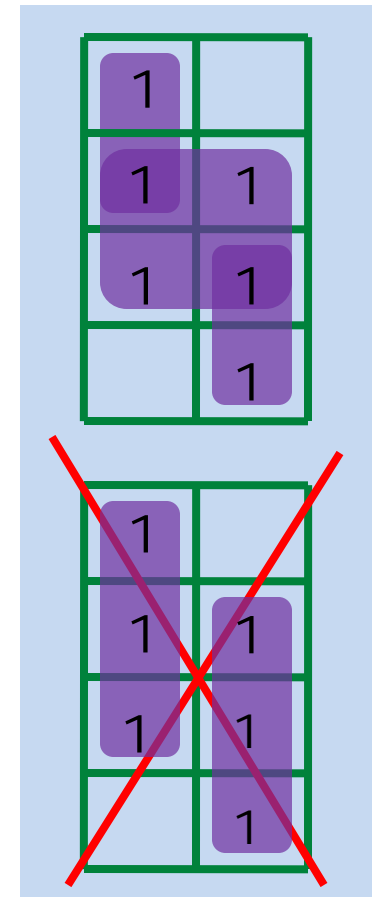- Aim is to group together adjacent cells containing as many ones as possible according to the following rules
 1. Groups **may not contain** any cell containing a zero
 2. Groups may be **horizontal or vertical** but **not diagonal**
 3. Groups **must contain** either **1,2,4** or **8** cells
 4. Groups **may overlap**



Karnaugh Mapping

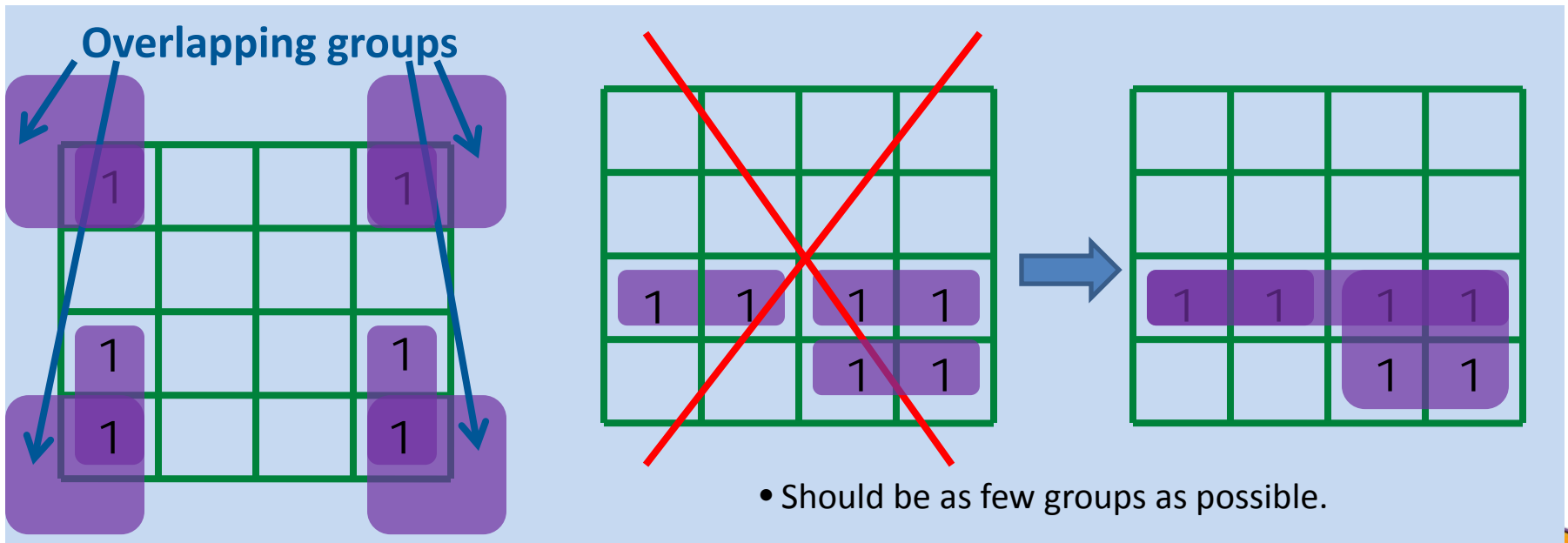5. Each cell **must contain a one** must be in at least one group
6. Groups (at the edges) **may wrap around** the table
7. There should be **as few groups as possible**



Karnaugh Mapping

- Now let's try another example. Write it in C++ code
 - $X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$



Karnaugh Mapping

- Now let's try another example. Write it in C++ code

$$- X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B				
AB	1			1
AB'	1	1	1	1



Karnaugh Mapping

- Now let's try another example. Write it in C++ code
 - $X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B				
AB	1			1
AB'	1	1	1	1



Karnaugh Mapping

- Now let's try another example. Write it in C++ code
 - $X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B				
AB	1			1
AB'	1	1	1	1



Karnaugh Mapping

- Now let's try another example. Write it in C++ code
 - $X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B				
AB	1			1
AB'	1	1	1	1



Karnaugh Mapping

- Now let's try another example. Write it in C++ code
 - $X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B				
AB	1			1
AB'	1	1	1	1



Karnaugh Mapping

- Now let's try another example. Write it in C++ code too.
 - $X = A'B'C' + AC'D' + AB' + ABCD' + A'B'C$

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B				
AB	1			1
AB'	1	1	1	1

- Final Equation is $X = B' + AD'$
- In C++, $X = !B \ || \ (A \ \&\& \ !D)$



Lecture 6

Boolean Logic & Logic Gates III

NAND LOGIC




NAND Gate Logic

- **1 of 2** basic logic gates from which any other gates can be constructed
 - Which is the other?
- These are sometimes called “**universal gates**”
 - However modern integrated circuits **aren't solely** made up of just NAND or NOR gates
 - i.e. for CPU design, full custom designs (transistor level) necessary to **maximise performance**




Using NAND to express NOT

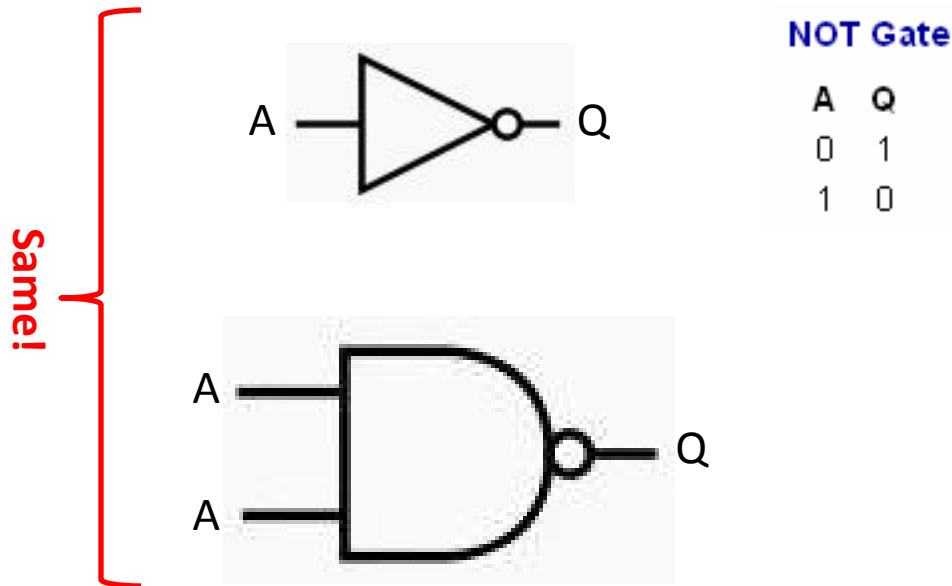
- NAND can be used to express other gate types
- Example:




Using NAND to express AND

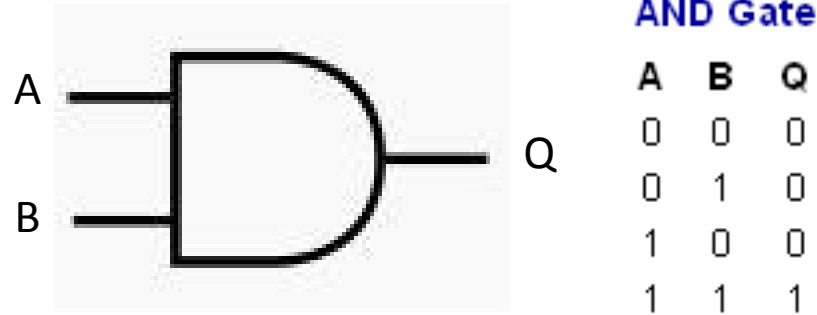

Same as

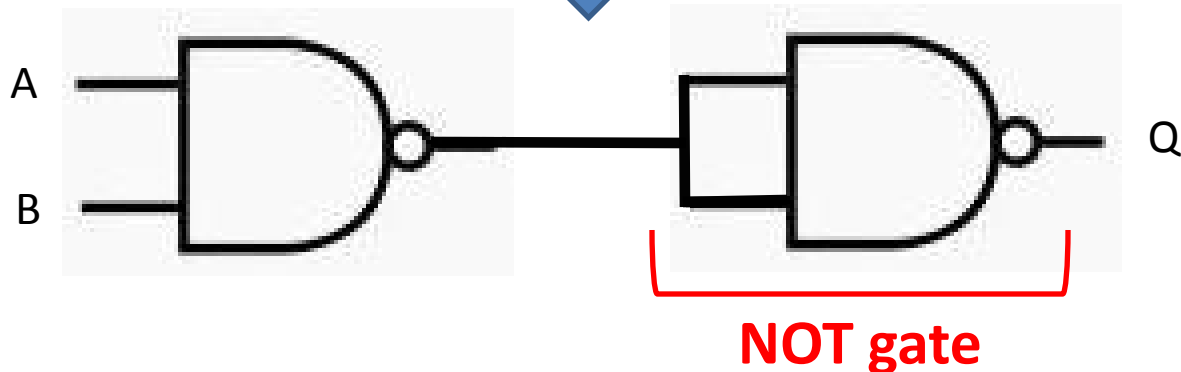


Using NAND to express OR

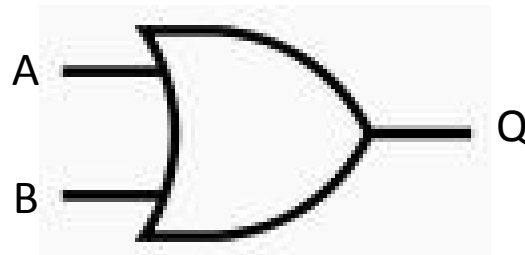

OR Gate


A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

Recall from DeMorgan's theorem

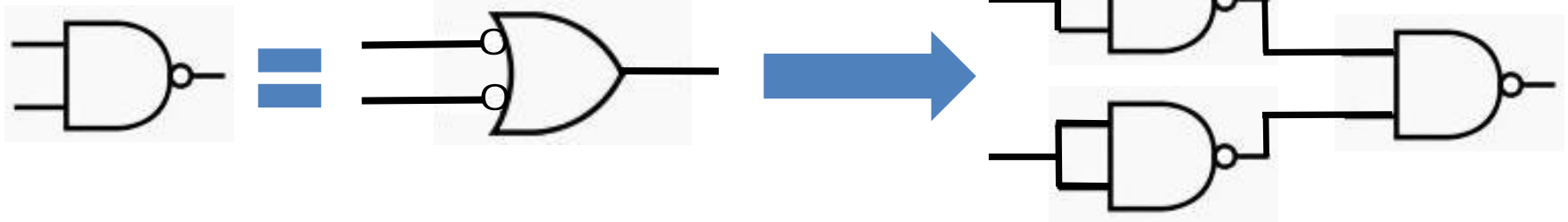

Using NAND to express NOR

- NOR = **OR + NOT**

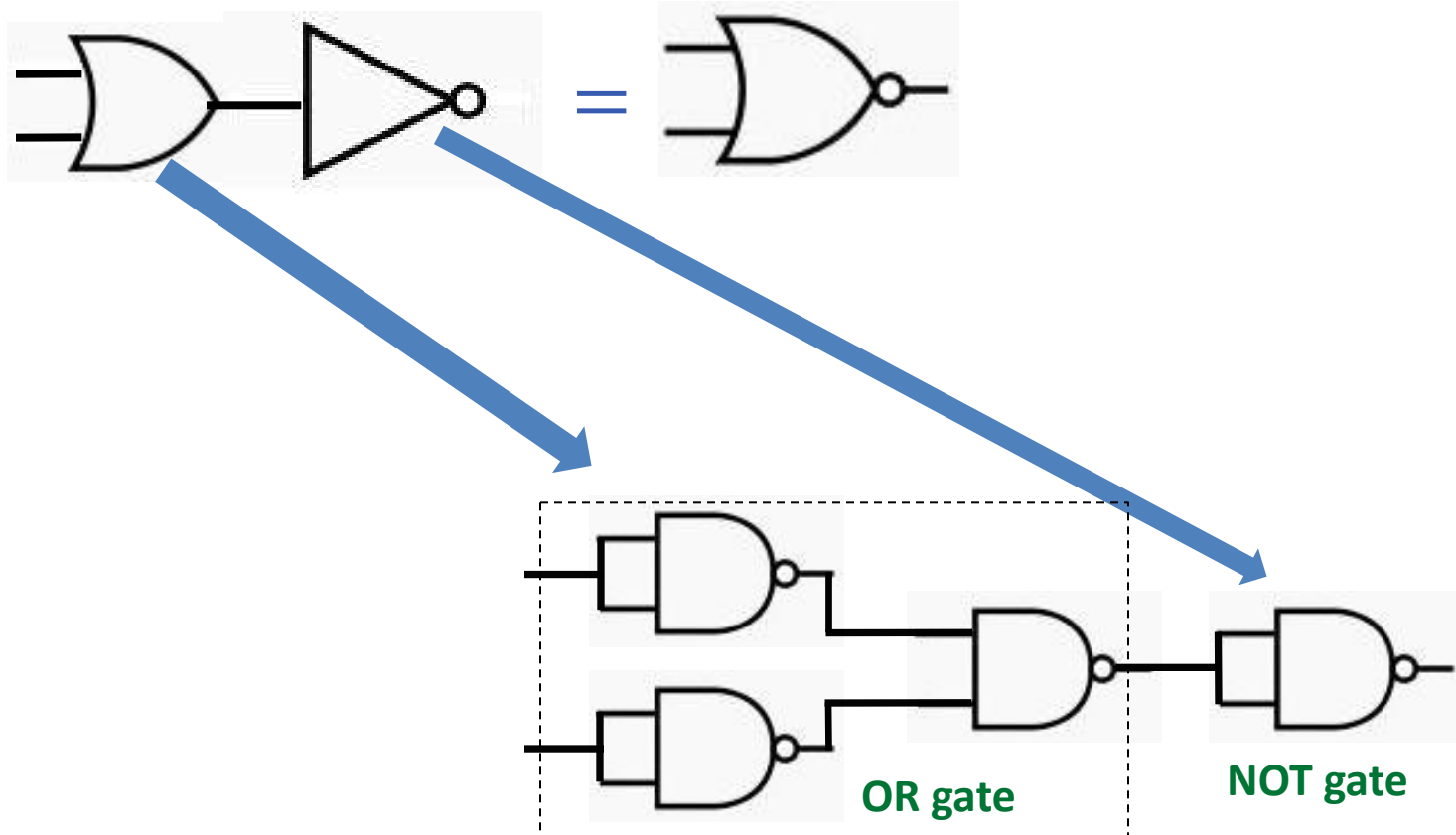

XOR & XNOR

- NAND can also express logic for **XOR or XNOR** gate
- Do some research online to find out how!



Lecture 7

Boolean Logic & Logic Gates III

BCD NOTATION




About BCD Notation

- Binary Coded Decimal Notation
 - Method of **encoding a decimal number** by **swapping** its digits for the **binary equivalent**

– Example:

9356 (Decimal)

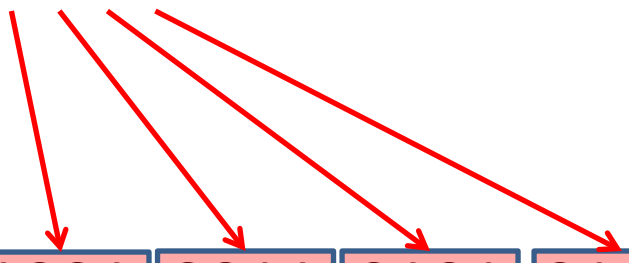= **1001** **0011** **0101** **0110** (BCD)



Decimal Digit	Binary
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001



New Things Next Time

- End of Data Representation, Digital Logic, and Logic Gates
- Questions?

