

# Boolean Logic & Logic Gates II

## Lecture 5



## Lecture 5

### Boolean Logic & Logic Gates

# BOOLEAN ALGEBRA



# Boolean Algebra

- Logical Calculus of truth values
- Developed by George Boole in 1840s
- Algebra of only 2 values
  - 0 and 1
  - True and False



# Boolean Algebra

- Resembles algebra of real number
- Instead of multiplication, addition and negation, it is replaced by logical operations of
  - conjunction  $x \wedge y$  ( **AND** ),
  - disjunction  $x \vee y$  ( **OR** ), and
  - negation  $\neg x$  ( **NOT** )



# Algebra of Real Numbers

- Commutative Law of Addition and Commutative Law of Multiplication:
  - $A + B = B + A$
  - $AB = BA$
- Associative Law of Addition:
  - $(A + B) + C = A + (B + C)$
- Distributive Law
  - $A(B + C) = AB + AC$
  - $(A + B)(C + D) = AC + AD + BC + BD$

You should already know this from secondary school algebra.



# Boolean Algebra

- Commutative Law of Addition and Commutative Law of Multiplication:

- $A \vee B = B \vee A$

- $A \wedge B = B \wedge A$

- Associative Law of Addition:

- $(A \vee B) \vee C = A \vee (B \vee C)$

- $(A \wedge B) \wedge C = A \wedge (B \wedge C)$

- Distributive Law

- $A \wedge (B \vee C) = (A \wedge B) \vee (A \wedge C)$

- $A \vee (B \wedge C) = (A \vee B) \wedge (A \vee C)$

- $(A \vee B) \wedge (C \vee D) = (A \wedge C) \vee (A \wedge D) \vee (B \wedge C) \vee (B \wedge D)$

- $(A \wedge B) \vee (C \wedge D) = (A \vee C) \wedge (A \vee D) \wedge (B \vee C) \wedge (B \vee D)$

Boolean algebra is similar to real number algebra. Compare with the slide on the previous page





# Other Laws

- Annulment Law

- $A \cdot 0 = 0$



- $A + 1 = 1$

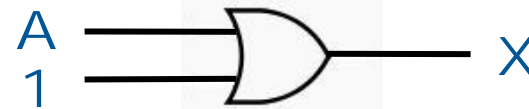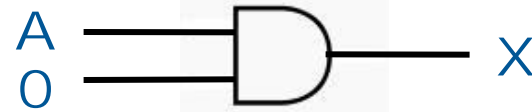

- Identity Law

- $A + 0 = A$

- $A \cdot 1 = A$

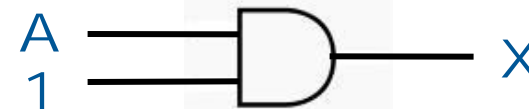
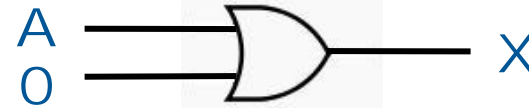


# Other Laws

- Indempotent Law

- $A + A = A$



- $A \cdot A = A$

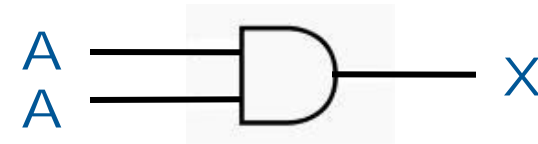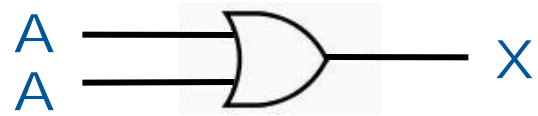

- Complement Law

- $A \cdot \overline{A} = 0$

- $A + \overline{A} = 1$

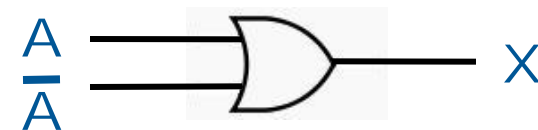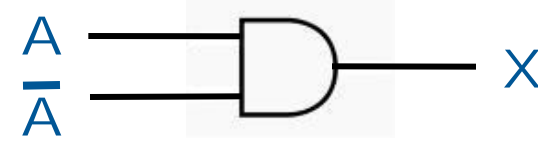




# Other Laws

- Double Negation Law

$$\overline{\overline{A}} = A$$

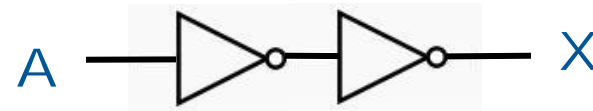

- You can also write negation as

$$\neg A$$

$$\sim A$$



# Example

- $Q = (A + B)(A + C)$   
 $= AA + AC + AB + BC$   
 $= A + AC + AB + BC$   
  
 $= A(1 + C) + AB + BC$   
 $= A.1 + AB + BC$   
  
 $= A(1 + B) + BC$   
 $= A.1 + BC$

$$Q = A + BC$$

Distributive law

Identity AND

law ( $A.A = A$ )

Distributive law

Identity OR

law ( $1 + C = 1$ )

Distributive law

Identity OR

law ( $1 + B = 1$ )

Identity AND law ( $A.1 = A$ )



# Example

- $Q = A + AB$   
 $= A(1+B)$   
 $= A(1)$   
 $= A$

Distributive law

Identity OR law ( $1 + B = 1$ )

- $Q = A + \neg AB$   
 $= A + AB + \neg AB$   
 $= A + B(A + \neg A)$   
 $= A + B(1)$   
 $= A + B$

See above example

Distributive law

Complement law



# Example

$$\begin{aligned}
 \bullet \quad Q &= (A \vee B) \wedge (A \vee C) \\
 &= (A \wedge A) \vee (A \wedge C) \vee (A \wedge B) \vee (B \wedge C) \\
 &= A \vee (A \wedge C) \vee (A \wedge B) \vee (B \wedge C)
 \end{aligned}$$

Distributive law

Identity AND

law ( $A \wedge A = A$ )

$$= (A \wedge (1 \vee C)) \vee (A \wedge B) \vee (B \wedge C)$$

Distributive law

$$= (A \wedge 1) \vee (A \wedge B) \vee (B \wedge C)$$

Identity OR

law ( $1 \vee C = 1$ )

$$= (A \wedge (1 \vee B)) \vee (B \wedge C)$$

Distributive law

$$= (A \wedge 1) \vee (B \wedge C)$$

Identity OR

law ( $1 \vee B = 1$ )

$$Q = A \vee (B \wedge C)$$

Identity AND

law ( $A \wedge 1 = A$ )



## Lecture 5

### Boolean Logic & Logic Gates II


# SIMPLIFICATION OF LOGIC CIRCUITS



# Simplification of Logic Circuits

- Boolean Algebra is used to simplify logic circuits. Simplification is very important for reduction of circuit cost, physical size, and gate/circuit failures


## Example: Warning buzzer

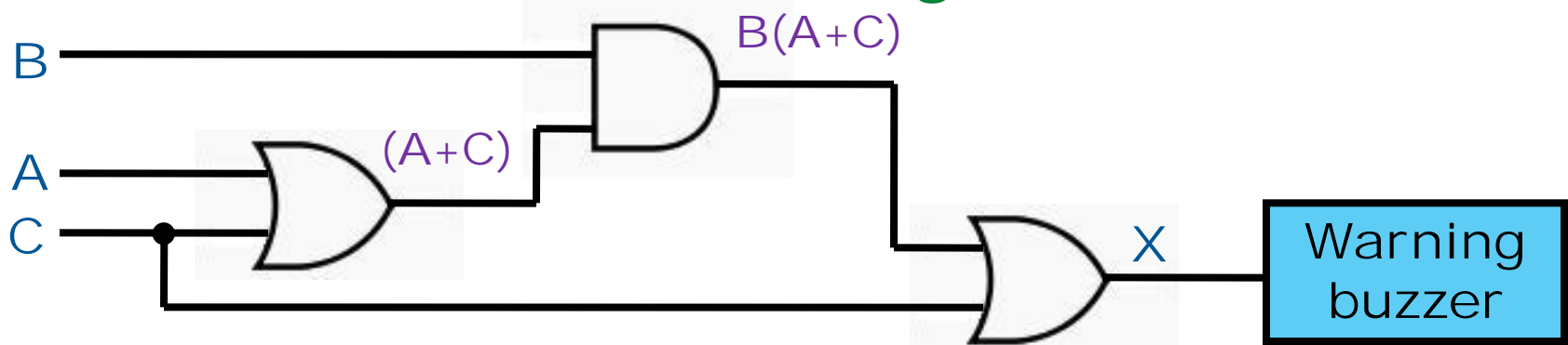

# Example: Warning Buzzer

- Equation:

$$X = B(A + C) + C$$

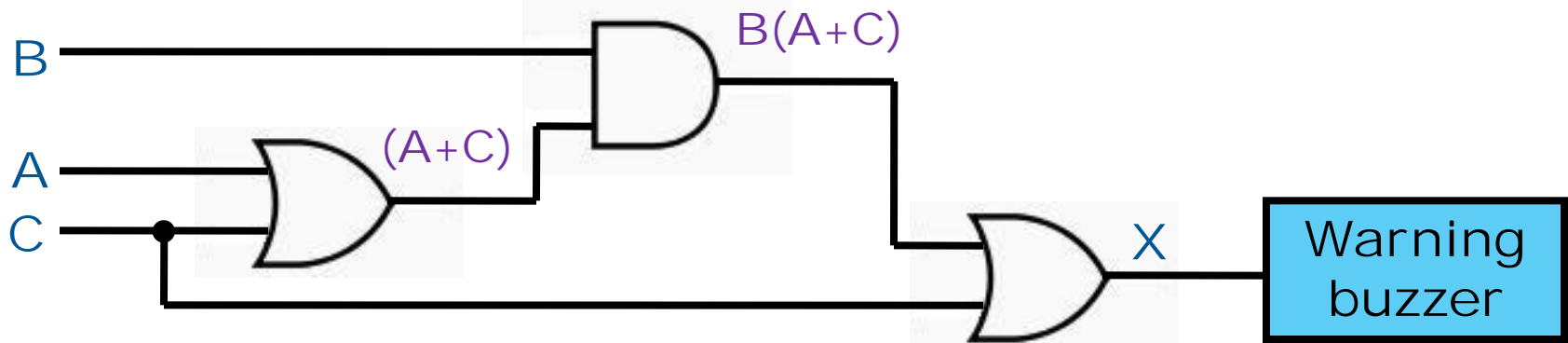

# Example: Warning Buzzer

- Let's Simplify

$$X = B (A + C) + C$$

Original Equation

$$X = BA + BC + C$$

**Distributive Law**

$$X = BA + BC + C.1$$

**Identity Law**

$$X = BA + C (B + 1)$$

**Distributive Law**

$$X = BA + C.1$$

**Identity Law**

$$X = BA + C$$

**Identity law**

$$X = AB + C$$


**Commutative Law**






# Example: Warning Buzzer

- Simplified

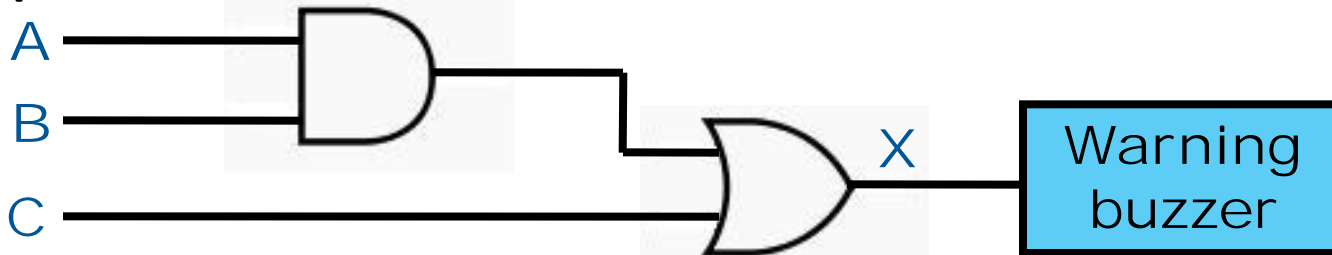


- Original

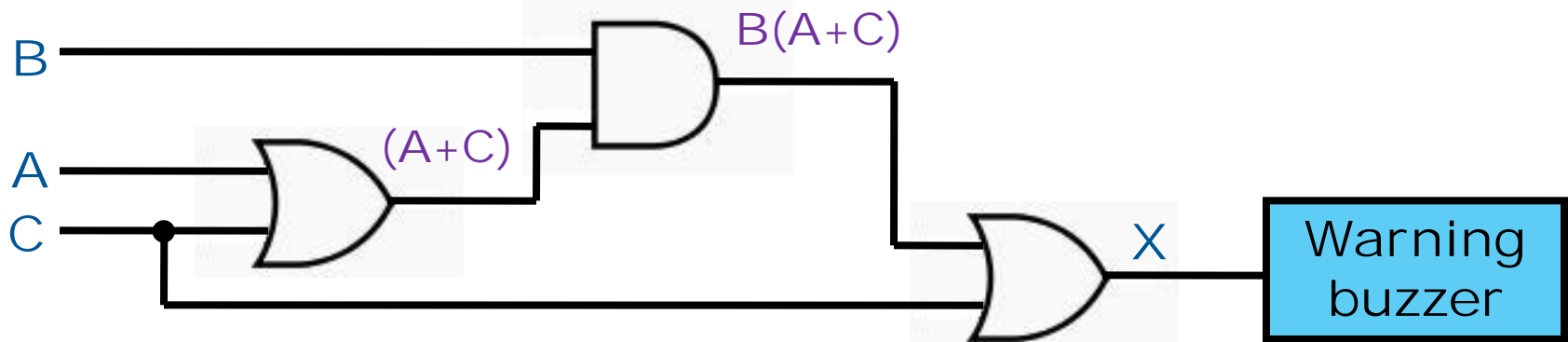


# Another Example

- What is the boolean equation?

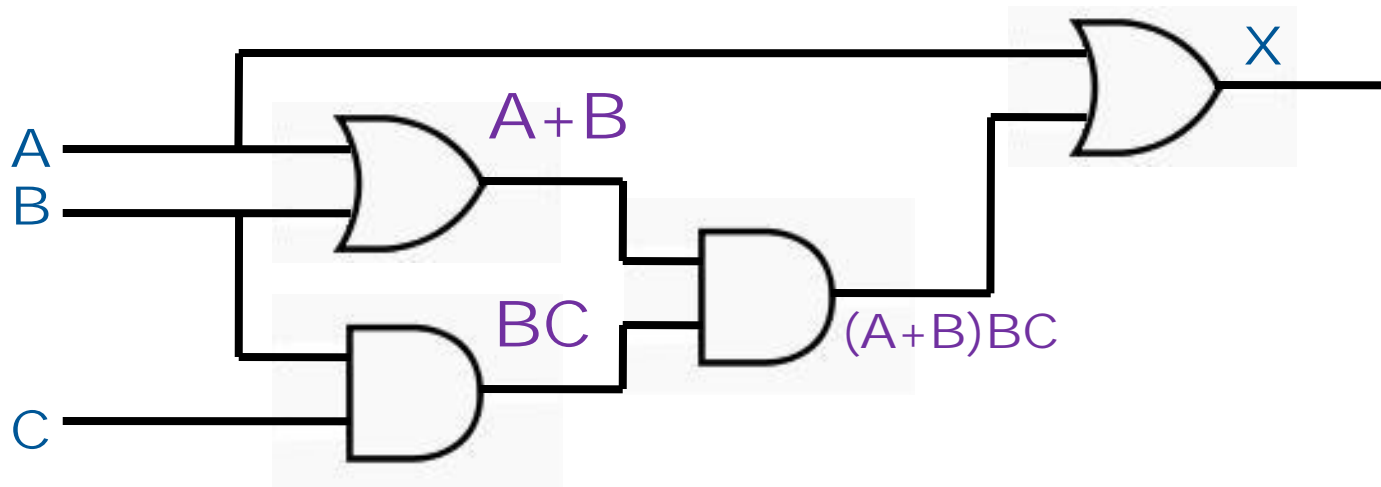

# Another Example

- $X = ((A + B) \cdot (B \cdot C)) + A = (A + B)BC + A$
- Or
  - $X = ((A \vee B) \wedge (B \wedge C)) \vee A$
- In C++
  - $X = ((A || B) \&\& (B \&\& C)) || A$

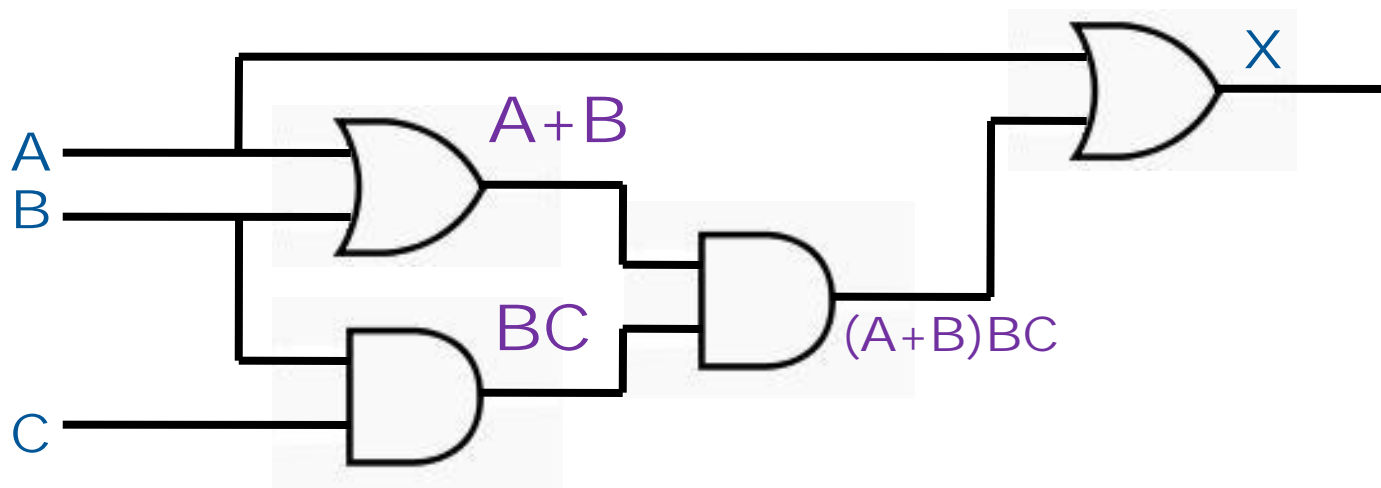

# Example

- Let's Simplify

$$X = (A + B)BC + A$$

$$X = \textcolor{red}{ABC} + \textcolor{red}{BBC} + A$$

$$X = ABC + \textcolor{blue}{BC} + A$$

$$X = ABC + \textcolor{blue}{BC.C} + A$$

$$X = \textcolor{red}{BC} (\textcolor{red}{A + 1}) + A$$

$$X = BC.\textcolor{green}{1} + A$$

$$\textcolor{green}{X} = \textcolor{green}{BC} + A$$

Original Equation

**Distributive Law**

**Idempotent Law**

**Idempotent Law**

**Distributive Law**


**Identity Law**

**Identity Law**



# Example

- Simplified logic circuit

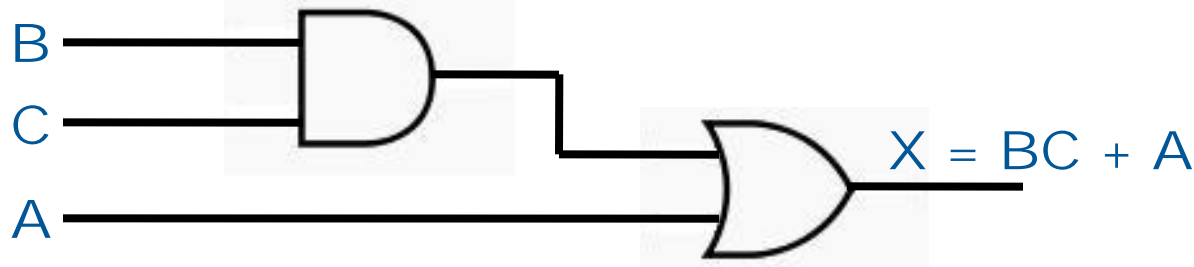

- In C++, the simplified Boolean Equation is:
  - $X = (B \&\& C) || A$
- Simplifying Boolean Equations in the program code makes it **more efficient** since there are **less conditions** for the CPU to check through



## Lecture 5

### Boolean Logic & Logic Gates II

# DEMORGAN'S THEOREM



# DeMorgan's Theorem

- Expressed in English:
  - The **negation** of a **conjunction** is the **disjunction** of the negations
  - The **negation** of a **disjunction** is the **conjunction** of the negations

$$\neg(P \wedge Q) \iff (\neg P) \vee (\neg Q)$$

$$\neg(P \vee Q) \iff (\neg P) \wedge (\neg Q)$$





# DeMorgan's Theorem

- States that  $\overline{A \cdot B} = \overline{A} + \overline{B}$  and  $\overline{A + B} = \overline{A} \cdot \overline{B}$
- For 3 or more variables:

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C} \quad \text{and} \quad \overline{A + B + C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$


As proof for 2 variables:

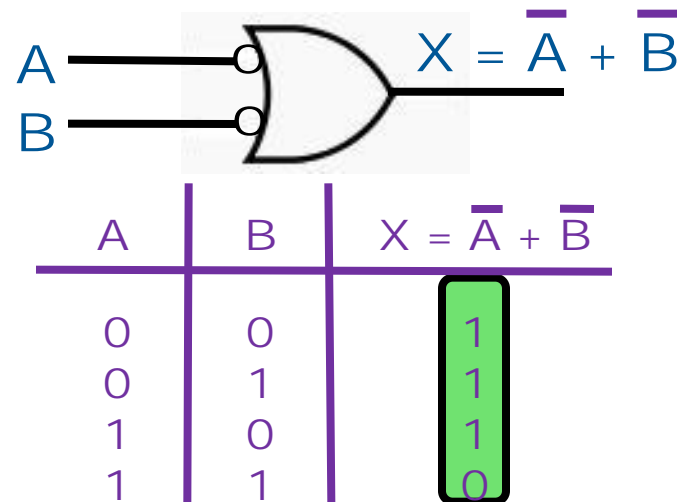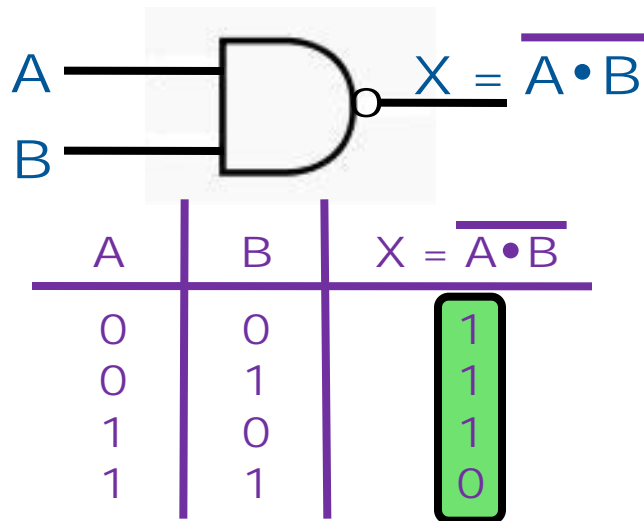




# DeMorgan's Theorem

- Gives us equivalent circuits

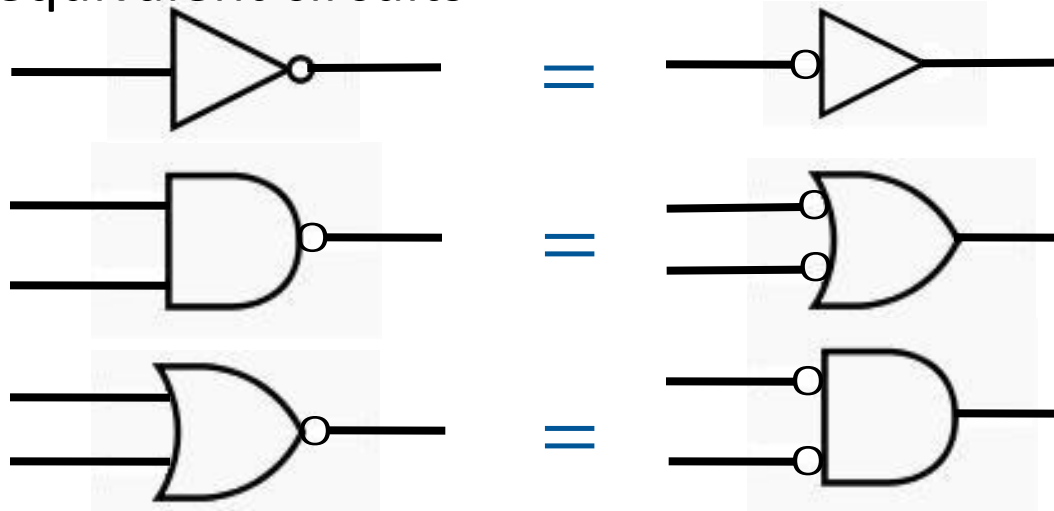


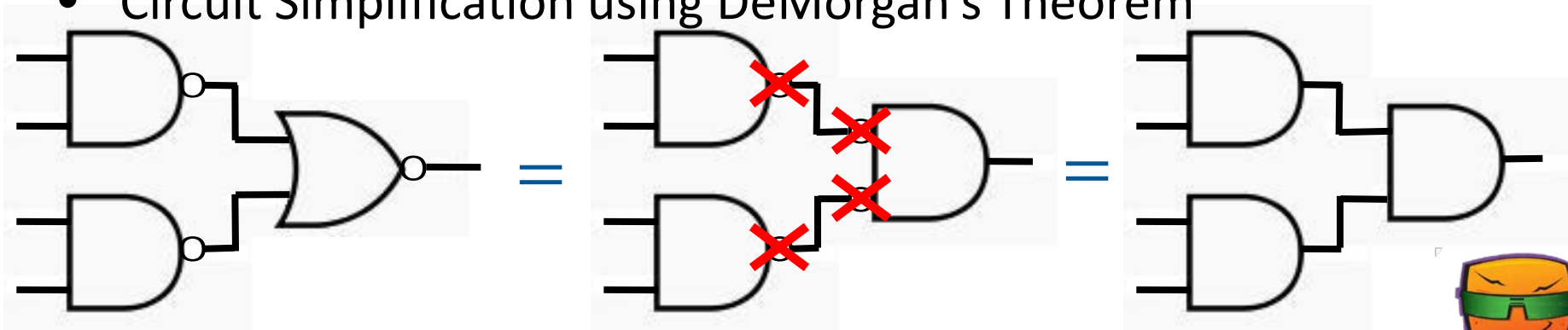- Circuit Simplification using DeMorgan's Theorem



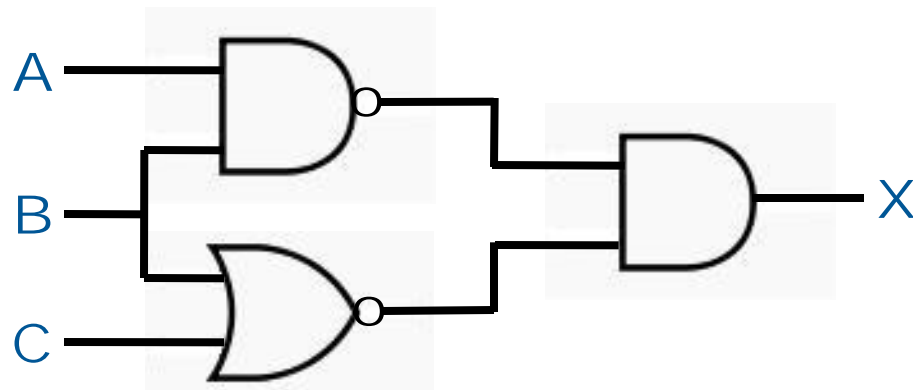
# Application of DeMorgan's Theorem

- Write the equation of the following circuit


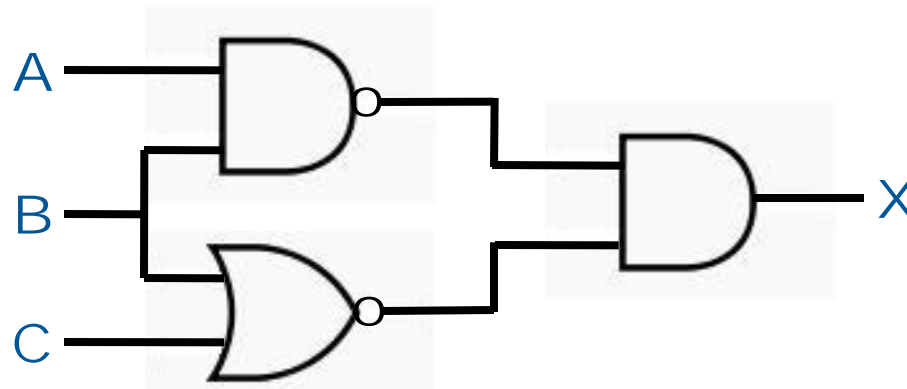
# Application of DeMorgan's Theorem

- Boolean Equation at X is:
  - $X = \overline{A}B \cdot (\overline{B} + C)$
- Apply DeMorgan's Theorem
  - $X = (\overline{A} + \overline{B}) \cdot (\overline{B} \cdot \overline{C})$



# Application of DeMorgan's Theorem

- Using Boolean Algebra

- $X = (\bar{A} + \bar{B}) \cdot \bar{B}\bar{C}$

- $X = \bar{A}\bar{B}\bar{C} + \bar{B}\bar{B}\bar{C}$

- $X = \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C}$

- $X = \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C} \cdot 1$

- $X = \bar{B}\bar{C}\bar{A} + \bar{B}\bar{C} \cdot 1$

- $X = \bar{B}\bar{C}(\bar{A} + 1)$

- $X = \bar{B}\bar{C}$

- $X = \neg \neg \bar{B}\bar{C}$

- $X = \neg (\bar{\bar{B}} + \bar{\bar{C}})$

- $X = \neg (B + C)$

Original Equation

**Distributive Law**

**Idempotent Law**

**Identity Law**

**Commutative Law**

**Distributive Law**

**Identity Law**

**Double Negation Law**


**DeMorgan's Theorem**

**Double Negation Law**




# Application of DeMorgan's Theorem

- Original ( $X = \bar{B}\bar{C}$ )

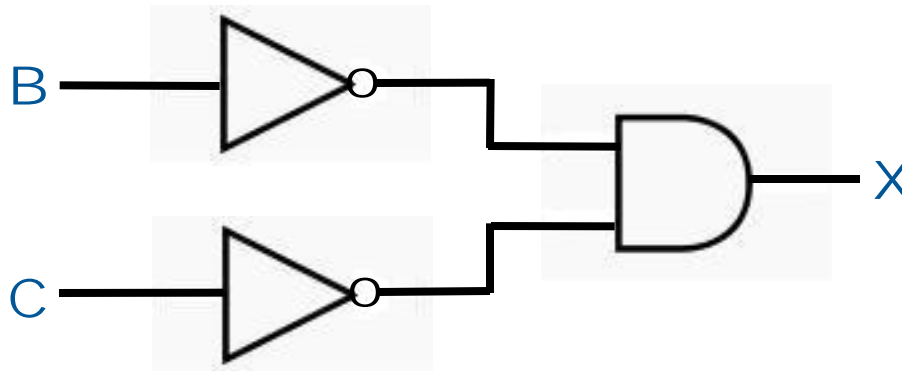

- Becomes  $X = \neg (B + C)$

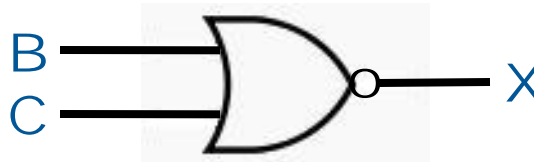

## Lecture 5

### Boolean Logic & Logic Gates II

# CONSTRUCTING A TRUTH TABLE




# Constructing a Truth Table

- We have this equation


$$X = \overline{A \cdot \overline{B}} + \overline{A \cdot (\overline{A} + C)}$$

- The logic circuit

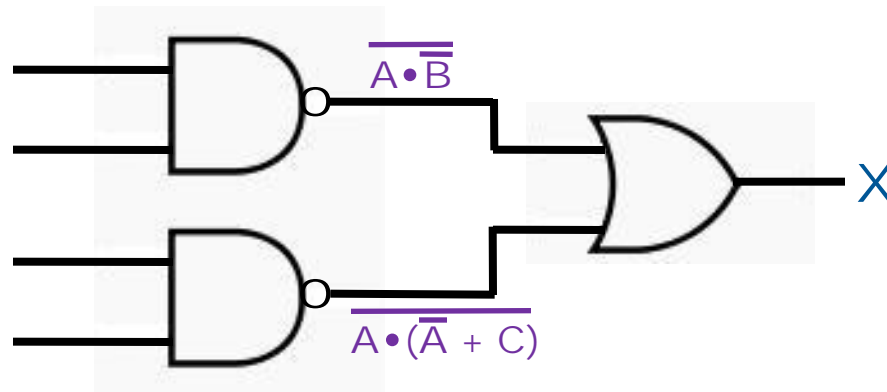

# Constructing a Truth Table

- Full Logic Circuit is:

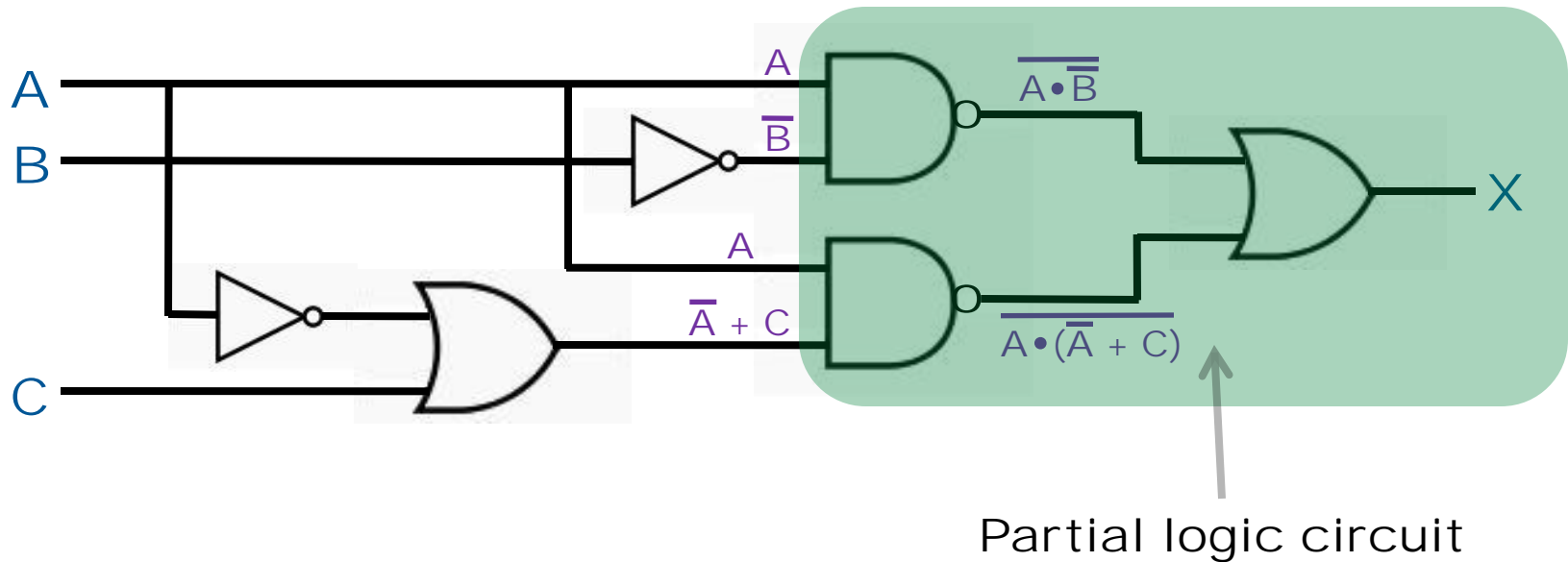



# Constructing a Truth Table

- Simply

$$X = \neg(A \neg B) + \neg(A(\neg A + C))$$

$$X = \neg A + \neg \neg B + \neg(A(\neg A + C))$$

$$X = \neg A + B + \neg(A(\neg A + C))$$

$$X = \neg A + B + (\neg A + \neg(\neg A + C))$$

$$X = \neg A + B + (\neg A + (\neg \neg A \neg C))$$

$$X = \neg A + B + (\neg A + A \neg C)$$

$$X = \neg A + \neg A + A \neg C + B$$

$$X = \neg A + A \neg C + B$$

Original Equation

DeMorgan's Theorem

Double Negation Law

DeMorgan's Theorem

DeMorgan's Theorem

Double Negation Law

Commutative Law

Idempotent Law

Continue next slide:



# Constructing a Truth Table

- Simply

$$X = \neg A + A\neg C + B$$

$$X = \neg( \neg\neg A, \neg( A\neg C ) ) + B$$

$$X = \neg( A, \neg( A\neg C ) ) + B$$

$$X = \neg( A ( \neg A + \neg\neg C ) ) + B$$

$$X = \neg( A ( \neg A + C ) ) + B$$

$$X = \neg( A\neg A + AC ) + B$$

$$X = \neg( 0 + AC ) + B$$

$$X = \neg( AC ) + B$$

$$X = \neg A + \neg C + B$$

Continued:

DeMorgan's Theorem

Double Negation Law

DeMorgan's Theorem

Double Negation Law

Distributive Law

Complement Law

Identity Law

DeMorgan's Theorem

Note:

.

$$A + \bar{A}B = A + B$$

and

$$\bar{A} + AB = \bar{A} + B$$



# Constructing the Truth Table

- Truth Table is:

A	B	C	$X = \overline{A} + \overline{C} + B$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$X = 1$  whenever  $A = 0$  OR  $C = 0$  OR  $B = 1$



## Lecture 5

### Boolean Logic & Logic Gates II


# DRAWING A TIMING DIAGRAM



# Drawing a Timing Diagram

- $X = AB + B\bar{C} + \bar{A}\bar{B}C$
- Truth table & Timing Diagram:

A	B	C	X
0	0	0	0
0	0	1	1 ← $\bar{A}\bar{B}C$
0	1	0	1 ← $B\bar{C}$
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1 ← $AB, B\bar{C}$
1	1	1	1 ← $AB$

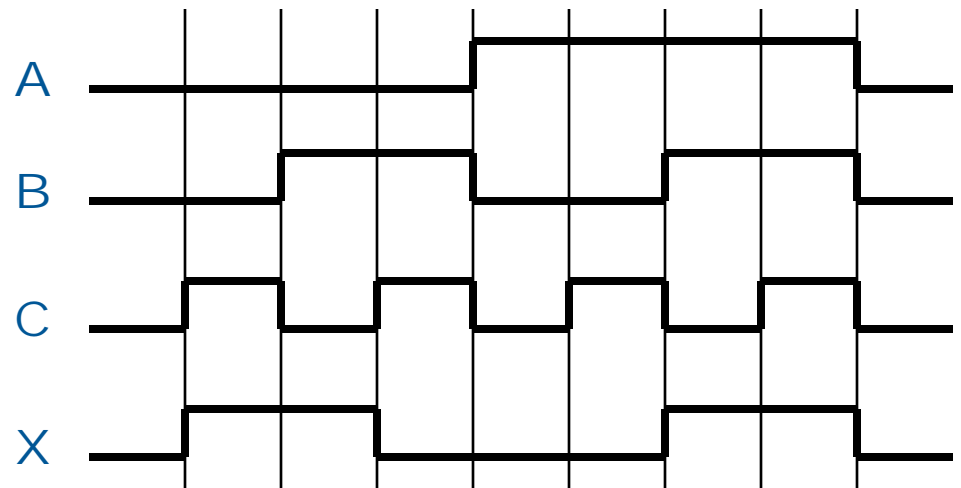

## Lecture 5


### Boolean Logic & Logic Gates II

# BUBBLE PUSHING


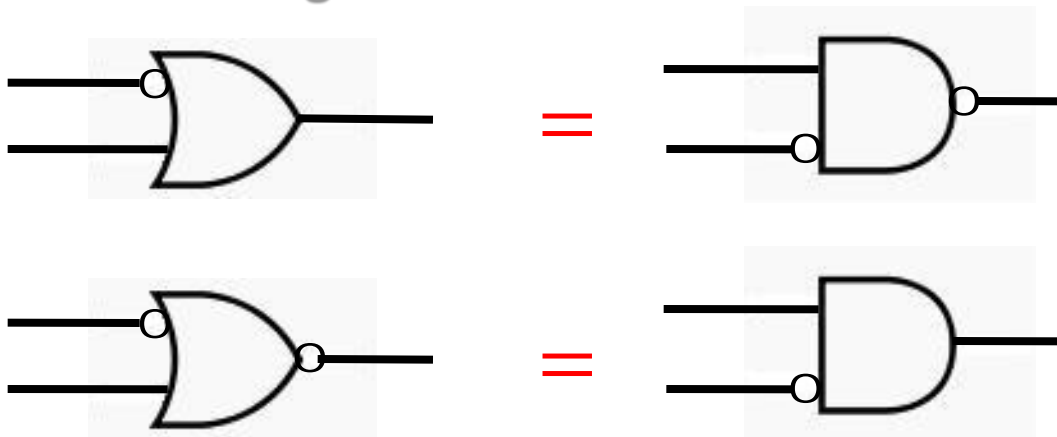
# Bubble Pushing

- Another trick to form an equivalent logic circuit is called bubble pushing.
- Based on DeMorgan's Theorem:
  - **Change** the logic gate between AND and OR
    - **AND to OR or**
    - **OR to AND**
  - **Add bubbles** to the input and outputs where there were **none**, and **remove** the **original** bubbles.



## Lecture 5

### Boolean Logic & Logic Gates II

# PRODUCT-OF-SUMS & SUM-OF-PRODUCTS





# Product-of-Sums & Sum-of-Products

- Most Boolean equations can be simplified into one of the following forms:
  - **Product-of-Sums** Expression (**POS**)
  - **Sum-of-Products** Expression (**SOP**)
- Example of **POS** expression
  - $X = ( \bar{B} + \bar{C} + D ) ( BC + \bar{E} )$
- Example of **SOP** expression
  - $X = A\bar{C}\bar{D} + \bar{C}D + B$



# Product-of-Sums & Sum-of-Products

- The **SOP** expression is **most often used** because it's **easy to figure out** truth tables, timing diagrams and Karnaugh maps
- We always strive to **simplify** a Boolean equation and then put it into the **SOP** form



# Example

- Filling out the truth table for

$$X = \neg( A \neg B + \neg CD )$$

$$= \neg( A \neg B ) \cdot \neg( \neg CD )$$

**DeMorgan's Theorem**

$$= ( \neg A + \neg \neg B ) \cdot ( \neg \neg C + \neg D )$$

**DeMorgan's Theorem**

$$= ( \neg A + B ) \cdot ( C + \neg D )$$

**Double Negation Law**

The above is the **POS** expression

Can you fill up the truth table from this form?



# Example

- What if convert it to SOP form

$$X = ( \neg A + B ) . ( C + \neg D )$$

- **Using distributive Law**

$$X = \neg AC + \neg A\neg D + BC + B\neg D$$

$$= \bar{A}C + \bar{A}\bar{D} + BC + B\bar{D} \leftarrow \text{SOP}$$

So to fill out the truth table,  
X = 1 whenever A = 0 **AND** C = 1;

**OR** A = 0 **AND** D = 0;

**OR** B = 1 **AND** C = 1;

**OR** B = 1 **AND** D = 0.



## Lecture 6

### Boolean Logic & Logic Gates III

# KARNAUGH MAPPING (TO BE CONTINUED)

